

# Ordinary Differential Equations

Barry Croke

Based on notes written by Lilia Ferrario (lilia@maths.anu.edu.au), June 2002

Semester 1, 2015

## Contents

<b>1</b>	<b>Laplace transforms: Systems of differential equations</b>	<b>2</b>
1.1	Application: Electrical network . . . . .	2

# 1 Laplace transforms: Systems of differential equations

## System of equations

In many applications, it often happens that one may have to solve a set of simultaneous linear differential equations. But we are lucky, because the Laplace transform method can be applied to solve systems.

So, consider:

$$\begin{aligned}y_1' &= a_{11}y_1 + a_{12}y_2 + g_1(t), \\y_2' &= a_{21}y_1 + a_{22}y_2 + g_2(t).\end{aligned}$$

Now if we indicate with  $Y_1 = \mathcal{L}\{y_1\}$ ,  $Y_2 = \mathcal{L}\{y_2\}$ ,  $G_1 = \mathcal{L}\{g_1\}$  and  $G_2 = \mathcal{L}\{g_2\}$ , then, since  $\mathcal{L}\{y'\} = sY - y(0)$ , we have:

$$\begin{aligned}sY_1 - y_1(0) &= a_{11}Y_1 + a_{12}Y_2 + G_1, \\sY_2 - y_2(0) &= a_{21}Y_1 + a_{22}Y_2 + G_2.\end{aligned}$$

Now collect the  $Y_1$  and  $Y_2$  terms:

$$\begin{aligned}(a_{11} - s)Y_1 + a_{12}Y_2 &= -y_1(0) - G_1 \\a_{21}Y_1 + (a_{22} - s)Y_2 &= -y_2(0) - G_2.\end{aligned}$$

Then solve for  $Y_1$  and  $Y_2$ . The solution is then obtained by taking the inverse Laplace transforms of  $Y_1$  and  $Y_2$ .

## 1.1 Application: Electrical network

### Electrical network

Find the currents  $i_1(t)$  and  $i_2(t)$  in the network shown in Figure 1 if  $L = 1$  henry,  $R = 50$  ohm,  $C = 10^{-4}$  farad,  $v(t) = 60$  volt, and the current is zero at  $t = 0$ .

As you can see, the current  $i_1(t)$  divides into currents  $i_2(t)$  and  $i_3(t)$  at the branch point  $A$ . Thus, Kirchhoff's current law says:

$$i_1(t) = i_2(t) + i_3(t).$$

Furthermore, we have to apply Kirchhoff's voltage law to each loop:

$$\begin{aligned}L \frac{di_1}{dt} + Ri_2 &= v(t) \\ \frac{1}{C} \int_0^t i_3(\tau) d\tau - Ri_2 &= 0.\end{aligned}$$

Differentiate the equation for the second loop with respect to time and get:

$$\begin{aligned}L \frac{di_1}{dt} + Ri_2 &= v(t) \\ \frac{i_3}{C} - Ri_2' &= 0.\end{aligned}$$

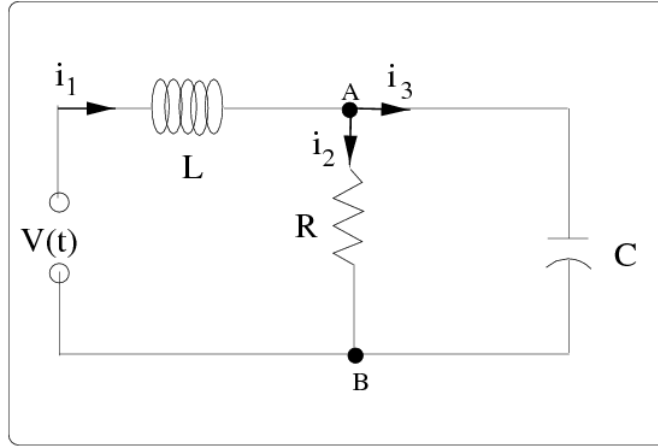


Figure 1: An electrical network

Since  $i_3(t) = i_1(t) - i_2(t)$ , then:

$$\begin{aligned} L \frac{di_1}{dt} + Ri_2 &= v(t) \\ \frac{i_1 - i_2}{C} - Ri_2' &= 0. \end{aligned}$$

By tidying things up we finally obtain:

$$\begin{aligned} Li_1' + Ri_2 &= v(t) \\ CRi_2' + i_2 - i_1 &= 0. \end{aligned}$$

Let's put the values in:

$$\begin{aligned} i_1' + 50i_2 &= 60 \\ 50i_2' + 10^4i_2 - 10^4i_1 &= 0. \end{aligned}$$

Now apply Laplace transform to each equation, remembering that  $i_1(0) = 0$  and  $i_2(0) = 0$ :

$$\begin{aligned} sI_1 + 50I_2 &= \frac{60}{s} \\ 50sI_2 + 10^4I_2 - 10^4I_1 &= 0. \end{aligned}$$

Collect  $I_1$  and  $I_2$ :

$$\begin{aligned} sI_1 + 50I_2 &= \frac{60}{s} \\ -200I_1 + (s + 200)I_2 &= 0. \end{aligned}$$

Now we have to solve for  $I_1$  and  $I_2$ .

From the second equation we find  $I_2 = 200I_1/(s + 200)$ . If we insert this in the first equation we get:

$$\begin{aligned} sI_1 + 50 \frac{200I_1}{s + 200} &= \frac{60}{s} \\ \Rightarrow I_1 &= \frac{60(s + 200)}{s^2(s + 200) + 10^4 s} \\ &= \frac{60s + 12,000}{s(s + 100)^2}. \end{aligned}$$

Decompose into partial fractions:

$$\begin{aligned} I_1 &= \frac{60s + 12,000}{s(s + 100)^2} \\ &= \frac{A}{s} + \frac{B}{s + 100} + \frac{C}{(s + 100)^2} \end{aligned}$$

which gives  $A = 6/5$ ,  $B = -6/5$  and  $C = -60$ .

$$I_1 = \frac{6/5}{s} - \frac{6/5}{s + 100} - \frac{60}{(s + 100)^2}.$$

Thus:

$$i_1(t) = \mathcal{L}^{-1}\{I_1(s)\} = \frac{6}{5} - \frac{6}{5}e^{-100t} - 60te^{-100t}.$$

For the last term, I have used the formula of differentiation of transforms  $\mathcal{L}\{tf(t)\} = -F'(s)$ , where, in our case,  $F(s) = -\frac{1}{s+100}$ .

Let's now find  $I_2$ . Since  $I_2 = 200I_1/(s + 200)$ , then

$$\begin{aligned} I_2 &= \frac{12,000}{s(s + 100)^2} \\ &= \frac{A}{s} + \frac{B}{s + 100} + \frac{C}{(s + 100)^2}. \end{aligned}$$

which gives  $A = 6/5$ ,  $B = -6/5$  and  $C = -120$ . Therefore:

$$I_2 = \frac{6/5}{s} - \frac{6/5}{s + 100} - \frac{120}{(s + 100)^2}.$$

Thus:

$$i_2(t) = \mathcal{L}^{-1}\{I_2(s)\} = \frac{6}{5} - \frac{6}{5}e^{-100t} - 120te^{-100t}.$$

Here I have used again, for the last term, the formula of differentiation of transform.

The current  $i_3(t)$  through the capacitor is given by  $i_1(t) - i_2(t)$ :

$$i_3(t) = 60te^{-100t}.$$

Note that

$$\lim_{t \rightarrow \infty} i_3(t) = 0.$$

The different current are shown in Figure 2.

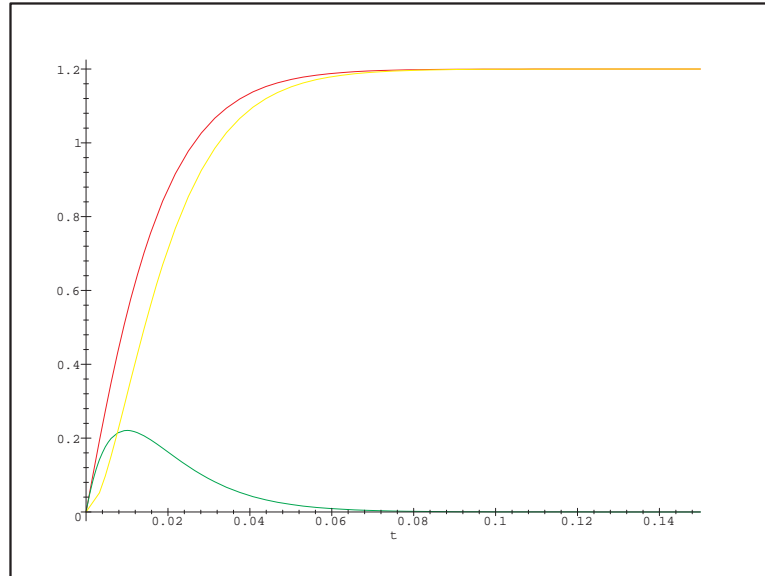


Figure 2: The currents  $i_1(t)$  (red),  $i_2(t)$  (yellow),  $i_3(t)$  (green) in the electrical network discussed in the text.